


( 3 Hours)

[ Total Marks : 80 ]


- N.B. : (1) Question No. 1 is compulsory.  
 (2) Attempt any three questions out of remaining five questions.  
 (3) Assume suitable data if required and mention the same in answer sheet.

1. Attempt any five questions :-

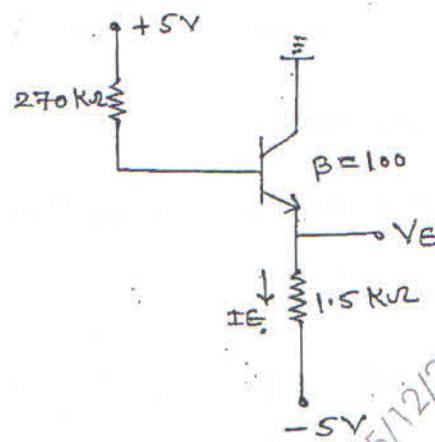- (a) Find  $V_E$  and  $I_E$  for the circuit given below.



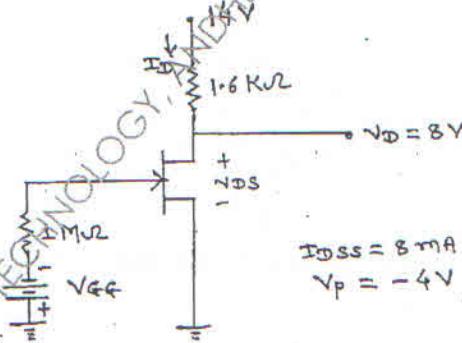
- (b) For the circuit given below find  $I_D$ ,  $V_{DS}$ ,  $V_{GS}$



- (c) Write down current equation of diode and explain significance of each parameters.  
 (d) Explain the concept of thermal runaway in BJT.

- 2 -

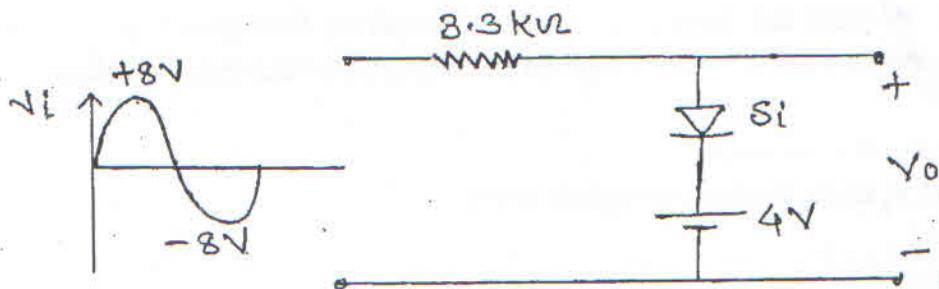
- (e) Draw the output Waveform  $V_o$  for circuit shown.



- (f) State and explain Barkhausen's criteria for oscillations.

2. (a) Determine Q-Print and draw d.c. load line for the amplifier shown.

10

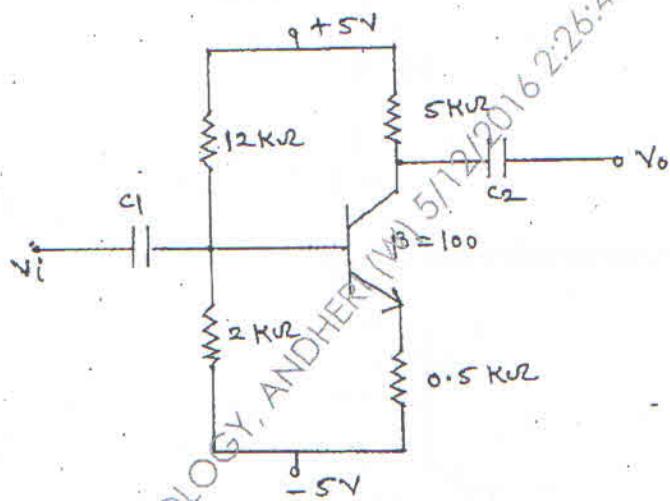

- (b) Derive the expression for frequency of oscillation for a BJT RC phase shift oscillator.

10

[ TURN OVER ]


**FW-Con. 9416-16.**

Sem II EXTC (CBGS)  
Analog Ele


QP Code : 30569

- 3 -

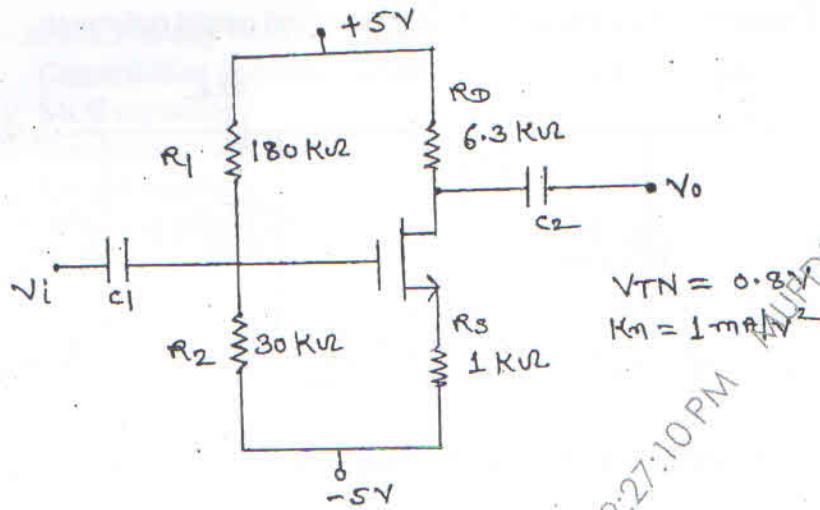3. (a) Determine voltage gain, Input resistance and output resistance for the MOSFET amplifier shown. 10



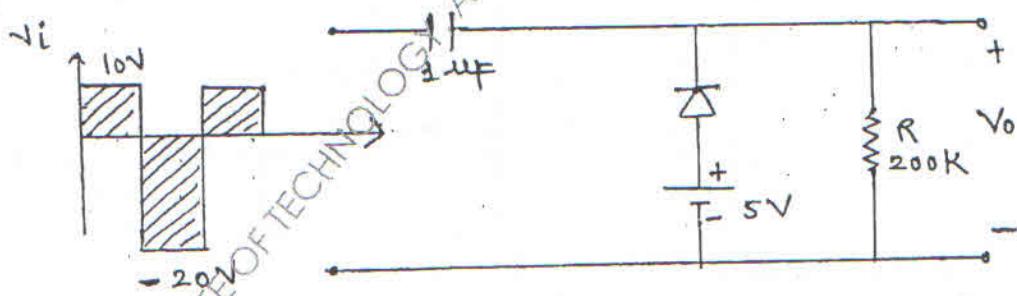
- (b) Explain the working and characteristics of n-channel Junction Field Effect Transistors (JFET) 10
4. (a) Draw the output waveform  $V_o$  for ckt shown if (i)  $V_r = 0V$  (ii)  $V_r = 0.7V$  where  $V_r$  is cutin voltage of diode 10




[ TURN OVER ]

- 4 -

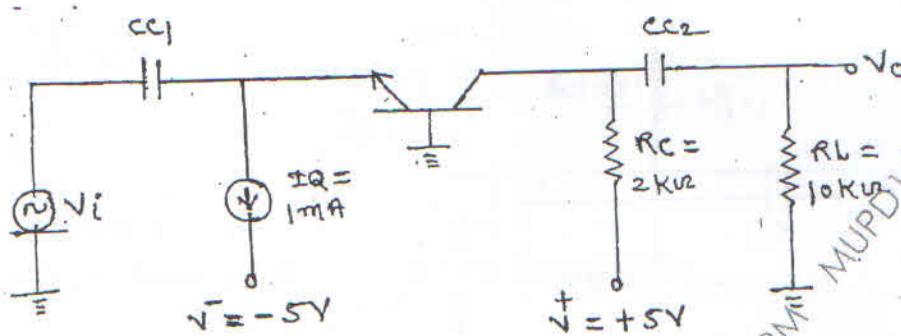- (b) For the common base circuit shown, the transistor has parameters  $\beta = 120$  and  $V_A = \infty$
- (i) Determine the quiescent  $V_{CEQ}$   
(ii) Determine the small signal voltage gain and output resistance.



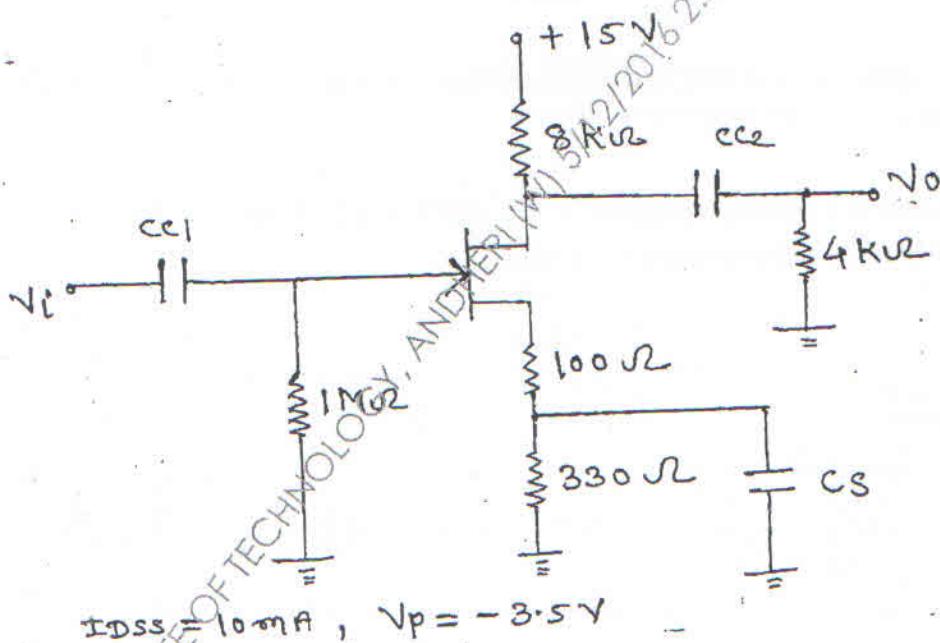5. (a) For the Amplifier shown determine (i) Q point (ii)  $A_v$ ,  $Z_i$ ,  $Z_o$



[ TURN OVER ]

Sem-II EXTC  
A.E.I

QP Code : 30569

- 5 -

- (b) Derive expressions for voltage gain, input resistance and output resistance for source follower circuit using n-channel MOSFET. 10
6. Write short notes on **any Four** :- 20
- (i) Construction and operation of varactor diode
  - (ii) MOS capacitor
  - (iii) Transistor as a switch
  - (iv) Crystal oscillator
  - (v) Hybrid- $\pi$  model of BJT

---

**EW-Con. 9416-16.**

MUPD16448 SARDAR PATEL INSTITUTE OF TECHNOLOGY, ANDHERI (W) 5/12/2016 2:27:57 PM MUPD16448 SARDAR PATEL INSTITUTE