

(3 hours)

Marks: 80

Note the following instructions.

1. Question No.1 is compulsory
2. Attempt any three questions from remaining five questions
3. Solve in total 4 questions
4. Assume suitable data wherever necessary, justify the same
5. Figures to the right indicate full marks.

1.a Realize the following symmetric function using full adders and gates. [5]
 $f(v, w, x, y, z) = S_{2,4}(v, w, x, y, z)$

1.b What is a Threshold logic element? Give its advantages and limitations [5]

1.c What is incompletely specified machines and how to specify using compatible states? [5]

1.d How to determine the state table of an unknown machine? [5]

2.a Use the Quine–McCluskey method to generate the set of essential prime implicants and to obtain the minimal expressions for the following functions. [10]

$$T(w, x, y, z) = \sum (0, 1, 2, 3, 5, 8, 10, 11, 13, 15)$$

2.b In the following state table, find the equivalence partition and the corresponding reduced machine in standard form. [10]


PS	NS, z	
	x = 0	x = 1
A	F, 0	B, 1
B	G, 0	A, 1
C	B, 0	C, 1
D	C, 0	B, 1
E	D, 0	A, 1
F	E, 1	F, 1
G	E, 1	G, 1

3.a (i) Give the properties of symmetric function. [10]

(ii) Decomposed the following function and determine the functions F and Φ .

$$f(v, w, x, y, z) = \sum (1, 2, 7, 9, 10, 17, 19, 26, 31) + \sum_{\phi} (0, 15, 20, 23, 25) \\ = F[\Phi(v, w, y), x, z]$$

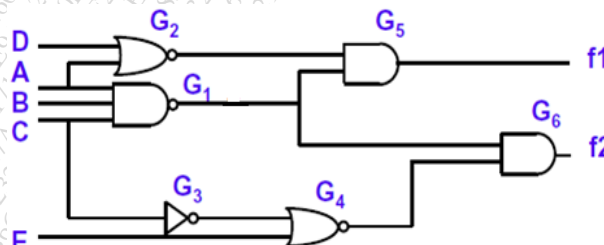3.b Find all the test vectors that detect faults s-a-0 and s-a-1 for all the input variable wires using the Fault table method. [10]




4.a Determine whether the following function is a threshold function, and if it is find a weight-threshold vector. [10]

$$f(v, w, x, y, z) = \sum (4, 7, 8, 11, 13, 14, 23, 27, 28, 29, 30)$$

4.b Explain homing and synchronizing sequence techniques [10]

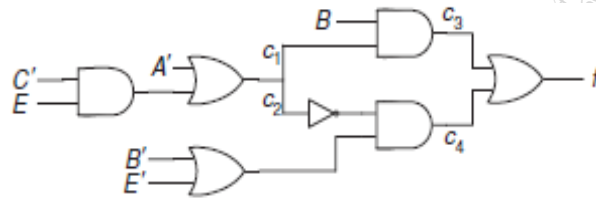5.a Find all the test vectors that detect input $A's-a-0$ by using the Path sensitization and the Boolean Differences method. [10]



5.b Explain the lattice of closed partitions of machine. [10]

6. a Design a one-input one-output synchronous sequential circuit (Mealy Machine) [10]
which produces an output symbol $z=1$, whenever the “1101” overlap input sequence occurs.(Use only J-K Flip flops)

6. b What are the components of ASM chart? Draw an ASM chart and state table for a [10]
2 bit up-down counter with mode control input.